

DIODE / TRANSISTORS

<https://github.com/teaksoon/lmaewapm>

BASIC DIODE:

Generally it is a device that allows current to flow in one direction, from +ve to -ve. If the diode is connected in reverse, electric current will not flow. There are many specialized diode with special features. For example: the "LED", which will glow when current flow through it. It comes in many shapes and sizes.



The diode markings with lines are normally the -ve side. If not sure, refer to product datasheet

Positive +ve Terminal
of Power Source (A)



Negative -ve Terminal (GND)
of Power Source (B)



(A) to (B) is
connected

Positive +ve Terminal
of Power Source (A)



Negative -ve Terminal (GND)
of Power Source (B)




(A) to (B) is
disconnected


BASIC TRANSISTORS:

A typical transistor allow and disallow current from flowing through it depending on the VOLTAGE at its BASE(B). Because of this ability, it is often used as a switch. Although there are other usage for transistors, we now only interested to use it as a switch.

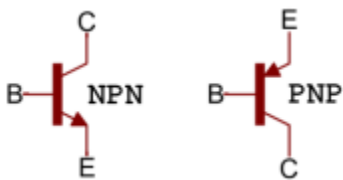They come in many shape and sizes. Below are some of the transistors that we normally see, there are many tiny ones inside our micro-controller chip that we cannot see. They are probably billions or trillions of transistors inside our modern computers chips, used for memory and logic operations.



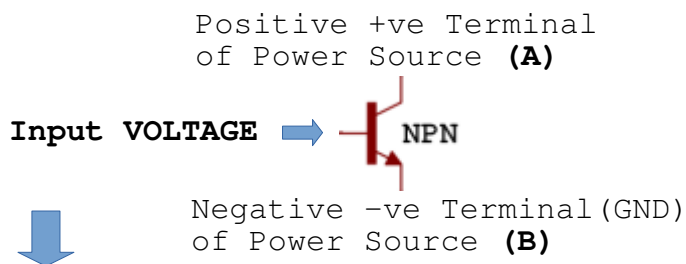
Transistor has 3 Pins. Refer to datasheet to find out which Pin is collector(C) or emitter(E) and the base(B) is normally in the middle.



When **Input VOLTAGE = 0V**, Path from (A) to (B) is **disconnected**

When **Input VOLTAGE is more than 0V**, Path from (A) to (B) is **connected**

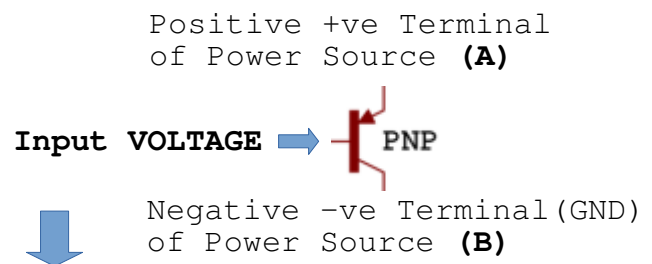(The actual minimum Input Voltage to trigger, refer to datasheet)



When **Input VOLTAGE = 0V**, Path from (A) to (B) is **connected**

When **Input VOLTAGE is more than 0V**, Path from (A) to (B) is **disconnected**

(The actual minimum Input Voltage to trigger, refer to datasheet)